

Switching Theory & Logic Design Laboratory
CSE Department, IIT Kharagpur
Spring Semester 2022-23

Module 1 : Combinational Logic Circuits

Assignment 3:

- (a) Design a 3-bit digital comparator using logic gates.
- (b) Design an 8-bit comparator using 4-bit comparator IC.

(1 day)